Multi-Pattern LED Generator Using Timers Counters and Logic Gates

Abstract - The purpose of this project is to design and build a pseudo-random multi-pattern LED chaser using only shift registers and basic sequential logic circuits. This model is unlike normal LED chasers that follow only a one fixed pattern. It can display multiple patterns and switch between them in a pseudo random way. The circuit is made using common ICs like shift registers, counters, multiplexers, logic gates and a 555 Timer. The 555 Timer generates clock pulses at regular intervals that control the lighting movement of LEDs while the counter decides which pattern of lighting will be followed at a particular instance. The multiplexer selects between lighting patterns. Some of the patterns the LEDs will follow are left shift, alternate blinking and converging pattern. Since the LEDs do no follow the same pattern every time, the display looks more interesting and dynamic. This project can be called an improvement over a standard LED chaser since it can produce many different lighting patterns instead of only one. It helps in a thorough understanding of the working of sequential logic circuits practically. Mainly this system can be used for decoration and display purposes and can also be used for educational demonstrations in digital electronics.

I. INTRODUCTION

Past LED chasers relied on simple counters or shift registers to light LEDs in a certain sequence, which tends to become repetitive and boring. This design aims to integrate shift registers, counters, multiplexers and logic gates to generate multiple lighting modes such as left-shift sequences, alternate blinking, converging and diverging effects with pseudo-random switching. Such a diverse display of lighting never gets boring and supports a wide range of applications at the same time.

The shift registers handle the sequential movement of LEDs. This ensures smooth transition of glowing LEDs across the system and circuit. The counters and logic circuit decide which pattern will be active at the particular instance while a multiplexer is used to switch between the different patterns.

To avoid predictability and repetitive pattern, a pseudo-random logic alters the order of patterns. This ensures that the LEDs behave differently each time the circuit runs.

The LED patterns is attractive and at the same time a good way to get into digital electronics, circuit designing and digital ICs and logic gates. Students learn about clock pulse generation, sequential logic, counting techniques, and control circuits. This project combines simplicity and sophistication. It is easy to build with basic ICs but at the same time generates complicated lighting patterns.

This random LED chaser or pattern generator is a realistic introduction to digital electronics and circuit designing. It allows creating simple ideas into a variety of possible outcomes to dive deep into the fundamentals of electronics while at the same time keep it educational, productive and modern.

II. PROPOSED WORK

With this project, we propose to design and implement an LED pattern generator using a variety of digital electronics components like NE555 timer and CD4017 decade counter. The NE555 timer is used to generate the clock pulse for the LEDs while the decade counter would activate the LED pattern and glow in the said sequence. Combining different logic gates and ICs allows to expand the project even further adding more lighting patterns and applying in other advanced and more dynamic projects.

The outputs of the decade counter can be connected and given to other ICs generating more diverse LED patterns and allowing multiple LEDs to glow simultaneously. The project showcases the real-life used of digital components like timers, counters, switches and combinational logic not only in digital electronics but other fields as well.

III. ARCHITECTURE

The proposed LED pattern generator can be divided into four major functional blocks: clock generation, counter and sequencing, logic-based pattern control and LED display.

1. Clock Generation Block

The NE555 timer IC is used in astable mode and generates the clock pulses. The frequency of these pulses is varied using the potentiometer allowing users to control the speed of the LED transitions.

2. Counter and Sequencing Block

The clock pulses output from the NE555 Timer is used as input for the CD4017 decade counter. The counter activates it output Q0-Q4 sequentially for every clock pulse generated. The outputs are what form the sequence for the LED pattern.

3. Pattern Control Block

The outputs of the decade counter are connected to 7432 OR gate and the SPST switches. The OR gate combines the multiple outputs from the counter to create a grouped LED pattern such as centre diverging transition enabling multiple LEDs to light up at once. The switches allow changing which pattern is generated.

4. LED Display Block

All these combined outputs are connected to 5 yellow LEDs each with a 220 Ω resistor. The LEDs glow according to the pattern being generated selected by the switches that are acting as selection lines.

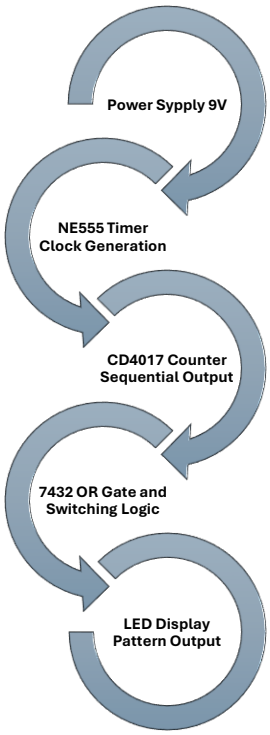


Fig: 1. System Architecture of the proposed LED Pattern Generator

IV. WORKING PRINCIPLE

A. Clock Generation Unit

The NE555 timer IC is the clock generating unit of the system which is operating in the astable mode. It generates continuous clock pules which are used to control the speed with which the LED pattern is generated. A potentiometer is added to adjust the frequency of the pulses allowing tuning of the pattern speed. The gives the user control over the speed with which subsequent LEDs glow.

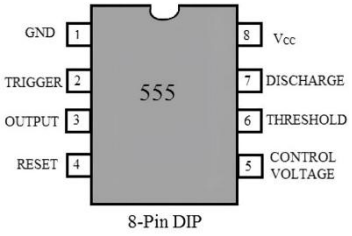


Fig: 2. NE555 Timer Pin Configuration

B. Sequential Pattern Generation

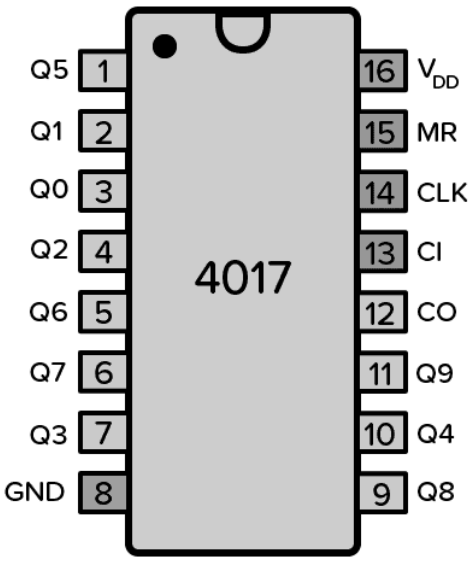


Fig: 2. CD4017 Decade Counter Pin Configuration

The CD4017 decade counter with ten decoded outputs. On each clock pulse, the high logic static shifts from one output pin to the next one.

For the left-to-right LED chaser:

- Q0 activates LED 1
- Q1 activates LED 2
- Q2 activates LED 3
- Q3 activates LED 4
- Q4 activates LED 5

Once the counter reaches the final output, the sequence resets and repeats.



Fig: 3. Default LED Pattern Sequence

C. 7432 Pattern Modification

The 7432 OR gate IC is used to combine different CD4017 outputs. This enables multiple LEDs to glow together and allows more advanced patterns.

- Q0 and Q4 ORed together to control LED1 and LED5
- Q1 and Q3 ORed together to control LED2 and LED4

D. Centre Diverging Pattern

The centre-diverging pattern creates a symmetrical visual effect. Instead of LEDs turning ON sequentially from one side to the other, the LEDs illuminate from the centre outward.

The proposed output is:

- LED3 ON
- LED2 and LED4 ON
- LED1 and LED5 ON

IV. COMPONENETS

Component	Value	Quantity
NE555 Timer	-	1
CD4017 Decade Counter	-	1
7432 OR Gate	-	1
SPST Switches	-	2
Potentiometer	10k	1
Power Supply	9V	1
LEDs	Yellow	5
Electrolytic Capacitor	10 µF	1
Ceramic Capacitor (104)	0.01 µF	
Resistors	220 Ω	5
Resistor	10 kΩ	1
Jumper Wires	-	-

V. EXPERIMENTAL RESULTS

The experimental results showed that the proposed circuit successfully generated multiple LED patterns using only hardware-based digital logic components. The left-to-right sequence operated correctly with each LED turning ON one after another according to the CD4017 output sequence. The centre-diverging pattern also functioned as expected, with LEDs glowing symmetrically from the middle toward the outer ends.

The NE555 timer produced stable clock pulses, and varying the potentiometer effectively changed the speed of LED transitions. At lower frequencies, the LED movement was clearly visible, while at higher frequencies, the display appeared smoother and more decorative.

The 7432 OR gates successfully combined multiple CD4017 outputs, allowing two LEDs to glow simultaneously and creating more advanced patterns. The switching mechanism also worked correctly, enabling easy transition between sequential and centre-diverging modes.

Overall, the experiment verified that multiple LED effects can be generated using counters, timers, and logic gates without requiring microcontrollers or programming.

VI. DISCUSSION

The system was able to generate different LED patterns using only digital ICs. The shift registers helped in creating smooth movement of LEDs, while the multiplexer circuit allowed the system to change automatically between different display patterns.

The output looked more interesting compared to a normal LED chaser due to the pseudo random pattern of selection of LED patterns. Since the active pattern keeps changing after a few clock pulses, the LEDs do not follow the same sequence all the time.

The speed of flow of LEDs can be changed by adjusting the speed of clock pulses. At slower speeds, the glow of each LED can be observed individually while at higher speeds, the LEDs serve a more decorative purpose.

The project demonstrates that creating visually appealing LED effects does not necessarily need microcontrollers or programming complex circuits. By using registers, counters, multiplexer and logic gates in the correct configuration, similar results can be achieved.

Nonetheless, the project is a strong way of showcasing the practical uses of sequential logic and digital electronics in the world. The project has scope to be expanded even further by integrating more ICs, adding LEDs, creating more patterns as well implementing other sensors like a sound-based control.

VI. COMPARIOSON

Parameter	Conventional	Proposed
Number of Patterns	Only one fixed pattern	Multiple patterns such as left-to-right, centre-diverging
Flexibility	Very limited	High flexibility due to switching and logic control
Components Used	Mostly timer and counter only	Timer, counter, OR gates, switches, and logic circuitry
Control Method	Fixed wiring	Selectable through switches and logic gates
Complexity	Simple	Moderately complex
Learning Outcome	Basic understanding of counters and timing	Better understanding of counters, logic gates, pattern control, and switching
Value	Low	High
Expandability	Difficult to expand	Can be expanded with more ICs, LEDs, and sensors
User Interaction	Minimal	User can switch between patterns and adjust speed
Speed Control	Limited	Adjustable using potentiometer
Application Scope	Simple LED chaser demonstrations	Decorative lighting, educational kits, display boards, and advanced LED projects

VII. CONCLUSION

The project objectives have been achieved allowing us to generate multiple patterns. The project has been successfully created using a NE555 Timer, CD4017 decade counter, logic gates and various LEDs. Different LED patterns like left to right running sequence were generated using the circuit setup. Adding logic gates and integrating with counters and switches creating more complex patterns without adding more LEDs, ICs etc.

We were able to successfully demonstrate the practical application of various digital electronics concepts including timing circuits, circuits designing, sequential logic, combinational logic all while also using counters and switching. It displays how simple ICs can be smartly combined and sequenced to generate complex output patterns. Overall, the project is low-cost, helps in grasping digital concepts and can be expanded into more complex projects to expand our horizons.

VII. REFERENCE

[1] Fundamentals of Digital Logic with Verilog Design, 3rd ed. New York, NY, USA: McGraw-Hill, 2014.

[2] Digital Electronics: Principles and Applications, 8th ed. New York, NY, USA: McGraw-Hill, 2013.

[3] Digital Design, 5th ed. Upper Saddle River, NJ, USA: Pearson, 2013.

[4] Texas Instruments, “NE555 Precision Timer Datasheet,” Dallas, TX, USA.

[5] Texas Instruments, “CD4017 Decade Counter Datasheet,” Dallas, TX, USA.

[6] Texas Instruments, “SN7432 Quad 2-Input OR Gate Datasheet,” Dallas, TX, USA.

[7] Digital Circuits. Pune, India: Technical Publications, 2015.

[8] Digital Electronics: An Introduction to Theory and Practice. New Delhi, India: PHI Learning, 2011.

[9] Modern Digital Electronics, 4th ed. New Delhi, India: Tata McGraw-Hill, 2009.

[10] Digital Principles and Applications, 8th ed. New York, NY, USA: McGraw-Hill, 2015.

[11] Electronic Devices and Circuit Theory, 11th ed. Upper Saddle River, NJ, USA: Pearson, 2013.

[12] Linear Integrated Circuits, 4th ed. New Delhi, India: New Age International, 2010.

[13] Op-Amps and Linear Integrated Circuits, 4th ed. New Delhi, India: Pearson, 2015.

[14] ON Semiconductor, “NE555 Timer IC Datasheet,” Phoenix, AZ, USA.

[15] Nexperia, “74HC4017 Decade Counter Datasheet,” Nijmegen, Netherlands.

[16] STMicroelectronics, “CD4017B Decade Counter/Divider Datasheet,” Geneva, Switzerland.

[17] Fairchild Semiconductor, “7432 Quad 2-Input OR Gate Datasheet,” San Jose, CA, USA.

[18] Microelectronic Circuits, 7th ed. New York, NY, USA: Oxford University Press, 2014.